

# Week No. 04

## Digital Logic Design

Nouman M Durrani

### BOOLEAN ALGEBRA

- Boolean algebra is the mathematics of digital systems. A basic knowledge of Boolean algebra is indispensable to the study and analysis of logic circuits.
- A variable is a symbol used to represent a logical quantity. Any single variable can have a 1 or a 0 value.
- The complement is the inverse of a variable and is indicated by a bar over the variable (overbar). For example,  
If  $A = 1$ , then  $\bar{A} = 0$ . If  $A = 0$ , then  $\bar{A} = 1$ .
- A literal is a variable or the complement of a variable.

# Laws of Boolean Algebra

- Commutative Laws The commutative law of addition for two variables is written as

$$A+B=B+A$$

- This law states that the order in which the variables are ORed makes no difference.

► **FIGURE 4-1**

Application of commutative law of addition.



The *commutative law of multiplication* for two variables is

$$AB = BA$$

This law states that the order in which the variables are ANDed makes no difference. Figure 4-2 illustrates this law as applied to the AND gate.

► **FIGURE 4-2**


Application of commutative law of multiplication.



**Associative Laws** The *associative law of addition* is written as follows for three variables:

$$A + (B + C) = (A + B) + C$$

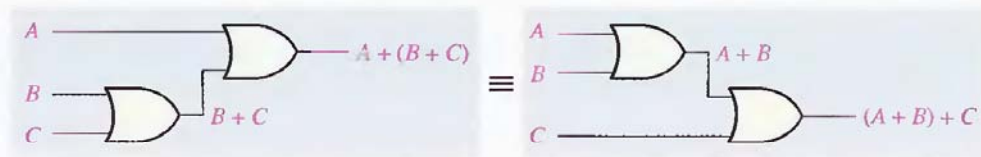
This law states that when ORing more than two variables, the result is the same regardless of the grouping of the variables. Figure 4-3 illustrates this law as applied to 2-input OR gates.



The *associative law of multiplication* is written as follows for three variables:

$$A(BC) = (AB)C$$

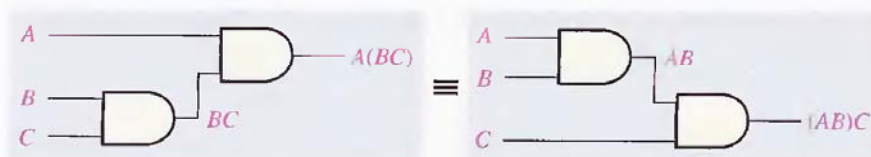
This law states that it makes no difference in what order the variables are grouped when ANDing more than two variables. Figure 4-4 illustrates this law as applied to 2-input AND gates.



**Distributive Law** The distributive law is written for three variables as follows:

$$A(B + C) = AB + AC$$

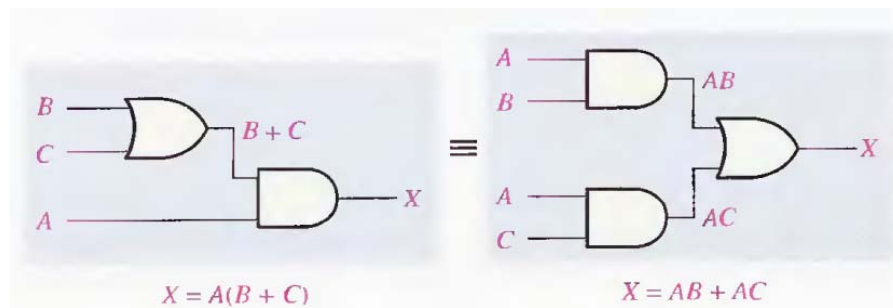This law states that ORing two or more variables and then ANDing the result with a single variable is equivalent to ANDing the single variable with each of the two or more variables and then ORing the products:



- |                      |                               |
|----------------------|-------------------------------|
| 1. $A + 0 = A$       | 7. $A \cdot A = A$            |
| 2. $A + 1 = 1$       | 8. $A \cdot \bar{A} = 0$      |
| 3. $A \cdot 0 = 0$   | 9. $\bar{\bar{A}} = A$        |
| 4. $A \cdot 1 = A$   | 10. $A + AB = A$              |
| 5. $A + A = A$       | 11. $A + \bar{A}B = A + B$    |
| 6. $A + \bar{A} = 1$ | 12. $(A + B)(A + C) = A + BC$ |

$A$ ,  $B$ , or  $C$  can represent a single variable or a combination of variables.

**TABLE 4-1**

Basic rules of Boolean algebra.

**Rule 11.  $A + \bar{A}B = A + B$**  This rule can be proved as follows:

$A + \bar{A}B = (A + AB) + \bar{A}B$	Rule 10: $A = A + AB$
$= (AA + AB) + \bar{A}B$	Rule 7: $A = AA$
$= AA + AB + A\bar{A} + \bar{A}B$	Rule 8: adding $A\bar{A} = 0$
$= (A + \bar{A})(A + B)$	Factoring
$= 1 \cdot (A + B)$	Rule 6: $A + \bar{A} = 1$
$= A + B$	Rule 4: drop the 1

A	B	$\overline{AB}$	$A + \overline{AB}$	$A + B$
0	0	0	0	0
0	1	1	1	1
1	0	0	1	1
1	1	0	1	1

↑ equal ↑

**Rule 12.**  $(A + B)(A + C) = A + BC$  This rule can be proved as follows:

$$\begin{aligned}
 (A + B)(A + C) &= AA + AC + AB + BC && \text{Distributive law} \\
 &= A + AC + AB + BC && \text{Rule 7: } AA = A \\
 &= A(1 + C) + AB + BC && \text{Factoring (distributive law)} \\
 &= A \cdot 1 + AB + BC && \text{Rule 2: } 1 + C = 1 \\
 &= A(1 + B) + BC && \text{Factoring (distributive law)} \\
 &= A \cdot 1 + BC && \text{Rule 2: } 1 + B = 1
 \end{aligned}$$

A	B	C	$A + B$	$A + C$	$(A + B)(A + C)$	$BC$	$A + BC$
0	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0
0	1	0	1	0	0	0	0
0	1	1	1	1	1	1	1
1	0	0	1	1	1	0	1
1	0	1	1	1	1	0	1
1	1	0	1	1	1	0	1
1	1	1	1	1	1	1	1

↑ equal ↑

## DEMORGAN'S THEOREMS

- DeMorgan's theorems provide mathematical verification of the equivalency of the NAND and negative-OR gates and the equivalency of the NOR and negative-AND gates.

**The complement of two or more ANDed variables is equivalent to the OR of the complements of the individual variables.**

The formula for expressing this theorem for two variables is

$$\overline{XY} = \overline{X} + \overline{Y}$$

Equation 4-6

DeMorgan's second theorem is stated as follows:

**The complement of a sum of variables is equal to the product of the complements of the variables.**

Stated another way,

**The complement of two or more ORed variables is equivalent to the AND of the complements of the individual variables.**


The formula for expressing this theorem for two variables is

$$\overline{X + Y} = \overline{X} \overline{Y}$$


Equation 4-7

Figure 4-15 shows the gate equivalencies and truth tables for Equations 4-6 and 4-7.

Figure 4–15 shows the gate equivalencies and truth tables for Equations 4–6 and 4–7.

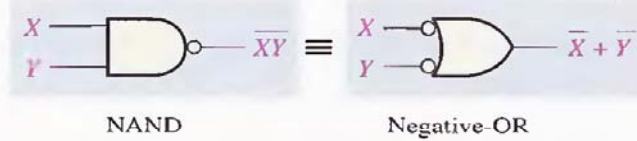

Inputs		Output	
X	Y	$\overline{XY}$	$\overline{X + Y}$
0	0	1	1
0	1	1	1
1	0	1	1
1	1	0	0

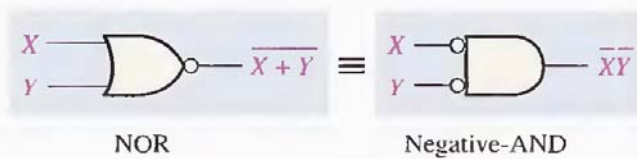

Inputs		Output	
X	Y	$\overline{X + Y}$	$\overline{XY}$
0	0	1	1
0	1	0	0
1	0	0	0
1	1	0	0

#### EXAMPLE 4–3

Apply DeMorgan's theorems to the expressions  $\overline{XYZ}$  and  $\overline{X + Y + Z}$ .

**Solution**

$$\overline{XYZ} = \overline{X} + \overline{Y} + \overline{Z}$$

$$\overline{X + Y + Z} = \overline{X} \overline{Y} \overline{Z}$$

**Related Problem** Apply DeMorgan's theorem to the expression  $\overline{\overline{X} + \overline{Y} + \overline{Z}}$ .

#### EXAMPLE 4–4

Apply DeMorgan's theorems to the expressions  $\overline{WXYZ}$  and  $\overline{W + X + Y + Z}$ .

**Solution**

$$\overline{WXYZ} = \overline{W} + \overline{X} + \overline{Y} + \overline{Z}$$

$$\overline{W + X + Y + Z} = \overline{W} \overline{X} \overline{Y} \overline{Z}$$

**Related Problem** Apply DeMorgan's theorem to the expression  $\overline{\overline{W} \overline{X} \overline{Y} \overline{Z}}$ .



### Applying DeMorgan's Theorems

The following procedure illustrates the application of DeMorgan's theorems and Boolean algebra to the specific expression

$$\overline{\overline{A + BC + D(E + F)}}$$

**Step 1.** Identify the terms to which you can apply DeMorgan's theorems, and think of each term as a single variable. Let  $A + BC = X$  and  $D(E + F) = Y$ .

**Step 2.** Since  $\overline{\overline{X + Y}} = \overline{X} \overline{Y}$ ,

$$\overline{\overline{(A + BC) + (D(E + F))}} = \overline{\overline{(A + BC)}} \overline{\overline{(D(E + F))}}$$

**Step 3.** Use rule 9 ( $\overline{\overline{A}} = A$ ) to cancel the double bars over the left term (this is not part of DeMorgan's theorem).

$$\overline{\overline{(A + BC)}} \overline{\overline{(D(E + F))}} = (A + BC) \overline{\overline{(D(E + F))}}$$

**Step 4.** Applying DeMorgan's theorem to the second term,

$$(A + BC) \overline{\overline{(D(E + F))}} = (A + BC) (\overline{\overline{D}} + \overline{\overline{E + F}})$$

**Step 5.** Use rule 9 ( $\overline{\overline{A}} = A$ ) to cancel the double bars over the  $E + \overline{F}$  part of the term.

$$(A + BC) (\overline{\overline{D}} + \overline{\overline{E + F}}) = (A + BC) (\overline{D} + E + \overline{F})$$

The following three examples will further illustrate how to use DeMorgan's theorems.

#### EXAMPLE 4-5

Apply DeMorgan's theorems to each of the following expressions:

(a)  $\overline{(A + B + C)D}$     (b)  $\overline{ABC + DEF}$     (c)  $\overline{AB + CD + EF}$

**Solution** (a) Let  $A + B + C = X$  and  $D = Y$ . The expression  $\overline{(A + B + C)D}$  is of the form  $\overline{XY} = \overline{X} \overline{Y}$  and can be rewritten as

$$\overline{(A + B + C)D} = \overline{A + B + C} \overline{D}$$

Next, apply DeMorgan's theorem to the term  $\overline{A + B + C}$ .

$$\overline{A + B + C} \overline{D} = \overline{A} \overline{B} \overline{C} \overline{D}$$

(b) Let  $ABC = X$  and  $DEF = Y$ . The expression  $\overline{ABC + DEF}$  is of the form  $\overline{X + Y} = \overline{X} \overline{Y}$  and can be rewritten as

$$\overline{ABC + DEF} = (\overline{ABC})(\overline{DEF})$$

Next, apply DeMorgan's theorem to each of the terms  $\overline{ABC}$  and  $\overline{DEF}$ .

$$(\overline{ABC})(\overline{DEF}) = (\overline{A} + \overline{B} + \overline{C})(\overline{D} + \overline{E} + \overline{F})$$

(c) Let  $AB = X$ ,  $CD = Y$ , and  $EF = Z$ . The expression  $\overline{AB + CD + EF}$  is of the form  $\overline{X + Y + Z} = \overline{X} \overline{Y} \overline{Z}$  and can be rewritten as

$$\overline{AB + CD + EF} = (\overline{AB})(\overline{CD})(\overline{EF})$$

Next, apply DeMorgan's theorem to each of the terms  $\overline{AB}$ ,  $\overline{CD}$ , and  $\overline{EF}$ .

$$(\overline{AB})(\overline{CD})(\overline{EF}) = (\overline{A} + \overline{B})(\overline{C} + \overline{D})(\overline{E} + \overline{F})$$

**Related Problem** Apply DeMorgan's theorems to the expression  $\overline{ABC + D + E}$ .

**EXAMPLE 4-6**

Apply DeMorgan's theorems to each expression:

(a)  $\overline{(\overline{A} + \overline{B}) + \overline{C}}$     (b)  $\overline{(\overline{A} + \overline{B}) + CD}$     (c)  $\overline{(A + B)\overline{CD} + E + \overline{F}}$

**Solution**

(a)  $\overline{(\overline{A} + \overline{B}) + \overline{C}} = \overline{(\overline{A} + \overline{B})}\overline{\overline{C}} = (A + B)C$

(b)  $\overline{(\overline{A} + \overline{B}) + CD} = \overline{(\overline{A} + \overline{B})}\overline{CD} = (\overline{\overline{A}}\overline{\overline{B}})(\overline{C} + \overline{D}) = \overline{AB}(\overline{C} + \overline{D})$

(c)  $\overline{(A + B)\overline{CD} + E + \overline{F}} = \overline{((A + B)\overline{CD})(E + \overline{F})} = (\overline{A}\overline{B} + C + D)\overline{EF}$

**Related Problem**

Apply DeMorgan's theorems to the expression  $\overline{AB}(C + \overline{D}) + E$ .

**EXAMPLE 4-7**

The Boolean expression for an exclusive-OR gate is  $\overline{A}B + A\overline{B}$ . With this as a starting point, use DeMorgan's theorems and any other rules or laws that are applicable to develop an expression for the exclusive-NOR gate.

**Solution**

Start by complementing the exclusive-OR expression and then applying DeMorgan's theorems as follows:

$$\overline{\overline{A}B + AB} = (\overline{\overline{A}B})(\overline{AB}) = (\overline{\overline{A}} + \overline{\overline{B}})(\overline{A} + \overline{B}) = (\overline{A} + B)(A + \overline{B})$$

Next, apply the distributive law and rule 8 ( $A \cdot \overline{A} = 0$ ).

$$(\overline{A} + B)(A + \overline{B}) = \overline{A}A + \overline{A}\overline{B} + AB + B\overline{B} = \overline{A}\overline{B} + AB$$

The final expression for the XNOR is  $\overline{A}\overline{B} + AB$ . Note that this expression equals 1 any time both variables are 0s or both variables are 1s.


**Related Problem**

Starting with the expression for a 4-input NAND gate, use DeMorgan's theorems to develop an expression for a 4-input negative-OR gate.

**TABLE 4-5**

Truth table for the logic circuit in Figure 4-16.

INPUTS				OUTPUT
A	B	C	D	$A(B + CD)$
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1

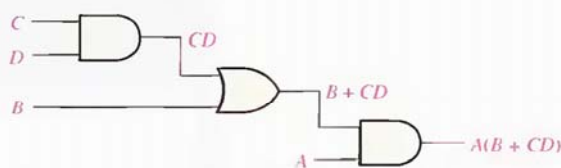

**FIGURE 4-16**

A logic circuit showing the development of the Boolean expression for the output.

Using Boolean algebra techniques, simplify this expression:

$$AB + A(B + C) + B(B + C)$$

**Solution** The following is not necessarily the only approach.

**Step 1:** Apply the distributive law to the second and third terms in the expression, as follows:

$$AB + AB + AC + BB + BC$$

**Step 2:** Apply rule 7 ( $BB = B$ ) to the fourth term.

$$AB + AB + AC + B + BC$$

**Step 3:** Apply rule 5 ( $AB + AB = AB$ ) to the first two terms.

$$AB + AC + B + BC$$

**Step 4:** Apply rule 10 ( $B + BC = B$ ) to the last two terms.


$$AB + AC + B$$

**Step 5:** Apply rule 10 ( $AB + B = B$ ) to the first and third terms.

$$B + AC$$

At this point the expression is simplified as much as possible. Once you gain experience in applying Boolean algebra, you can often combine many individual steps.

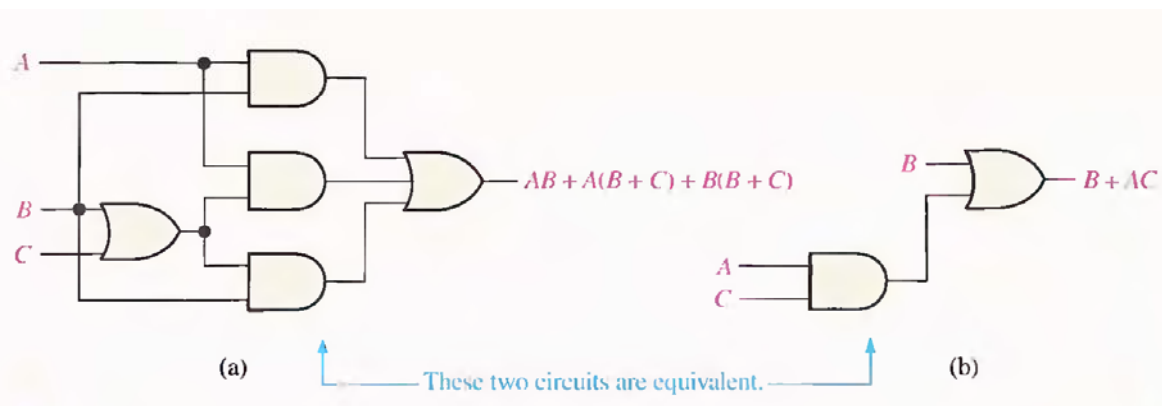**Related Problem** Simplify the Boolean expression  $\overline{A}\overline{B} + A(\overline{B} + \overline{C}) + B(\overline{B} + \overline{C})$ .





Simplify the following Boolean expression:

$$[\overline{A}B(C + BD) + \overline{A}\overline{B}]C$$

Note that brackets and parentheses mean the same thing: the term inside is multiplied (ANDed) with the term outside.

**Solution** Step 1: Apply the distributive law to the terms within the brackets.

$$(\overline{A}BC + \overline{A}BBD + \overline{A}\overline{B})C$$

Step 2: Apply rule 8 ( $\overline{B}B = 0$ ) to the second term within the parentheses.

$$(\overline{A}BC + A \cdot 0 \cdot D + \overline{A}\overline{B})C$$

Step 3: Apply rule 3 ( $A \cdot 0 \cdot D = 0$ ) to the second term within the parentheses.

$$(\overline{A}BC + 0 + \overline{A}\overline{B})C$$

Step 4: Apply rule 1 (drop the 0) within the parentheses.

$$(\overline{A}BC + \overline{A}\overline{B})C$$

Step 5: Apply the distributive law.

$$\overline{A}BCC + \overline{A}\overline{B}C$$

Step 6: Apply rule 7 ( $CC = C$ ) to the first term.

$$\overline{A}BC + \overline{A}\overline{B}C$$

Step 7: Factor out  $\overline{B}C$ .

$$\overline{B}C(A + \overline{A})$$

Step 8: Apply rule 6 ( $A + \overline{A} = 1$ ).

$$\overline{B}C \cdot 1$$

Step 9: Apply rule 4 (drop the 1).

$$\overline{B}C$$

**Related Problem** Simplify the Boolean expression  $[AB(C + \overline{BD}) + \overline{AB}]CD$ .

Simplify the following Boolean expression:

$$\overline{A}BC + \overline{A}\overline{B}\overline{C} + \overline{A}\overline{B}C + \overline{A}BC + ABC$$

**Solution** Step 1: Factor  $BC$  out of the first and last terms.

$$BC(\overline{A} + A) + \overline{A}\overline{B}\overline{C} + \overline{A}\overline{B}C + \overline{A}BC$$

Step 2: Apply rule 6 ( $\overline{A} + A = 1$ ) to the term in parentheses, and factor  $\overline{A}\overline{B}$  from the second and last terms.

$$BC \cdot 1 + \overline{A}\overline{B}(\overline{C} + C) + \overline{A}\overline{B}C$$

Step 3: Apply rule 4 (drop the 1) to the first term and rule 6 ( $C + \overline{C} = 1$ ) to the term in parentheses.

$$BC + \overline{A}\overline{B} \cdot 1 + \overline{A}\overline{B}C$$

Step 4: Apply rule 4 (drop the 1) to the second term.

$$BC + \overline{A}\overline{B} + \overline{A}\overline{B}C$$

Step 5: Factor  $\overline{B}$  from the second and third terms.

$$BC + \overline{B}(A + \overline{A}C)$$

Step 6: Apply rule 11 ( $A + \overline{A}C = A + \overline{C}$ ) to the term in parentheses.

$$BC + \overline{B}(A + \overline{C})$$

Step 7: Use the distributive and commutative laws to get the following expression:

$$BC + \overline{A}\overline{B} + \overline{B}C$$

Simplify the Boolean expression  $\overline{A}BC + \overline{A}\overline{B}C + \overline{A}BC + \overline{A}\overline{B}C$ .

Simplify the following Boolean expression:

$$\overline{AB} + \overline{AC} + \overline{A}BC$$

**Solution** **Step 1:** Apply DeMorgan's theorem to the first term.

$$(\overline{AB})(\overline{AC}) + \overline{A}BC$$

**Step 2:** Apply DeMorgan's theorem to each term in parentheses.

$$(\overline{A} + \overline{B})(\overline{A} + \overline{C}) + \overline{A}BC$$

**Step 3:** Apply the distributive law to the two terms in parentheses.

$$\overline{A}\overline{A} + \overline{A}\overline{C} + \overline{A}\overline{B} + \overline{B}\overline{C} + \overline{A}BC$$

**Step 4:** Apply rule 7 ( $\overline{A}\overline{A} = \overline{A}$ ) to the first term, and apply rule 10 [ $\overline{A}\overline{B} + \overline{A}BC = \overline{A}\overline{B}(1 + C) = \overline{A}\overline{B}$ ] to the third and last terms.

$$\overline{A} + \overline{A}\overline{C} + \overline{A}\overline{B} + \overline{B}\overline{C}$$

**Step 5:** Apply rule 10 [ $\overline{A} + \overline{A}\overline{C} = \overline{A}(1 + \overline{C}) = \overline{A}$ ] to the first and second terms.

$$\overline{A} + \overline{A}\overline{B} + \overline{B}\overline{C}$$

**Step 6:** Apply rule 10 [ $\overline{A} + \overline{A}\overline{B} = \overline{A}(1 + \overline{B}) = \overline{A}$ ] to the first and second terms.

$$\overline{A} + \overline{B}\overline{C}$$

**Related Problem** Simplify the Boolean expression  $\overline{AB} + \overline{AC} + \overline{A}BC$ .

## STANDARD FORMS OF BOOLEAN EXPRESSIONS

- All Boolean expressions can be converted into either of two standard forms: the sum-of-products form or the product-of-sums form.
- Standardization makes the evaluation, simplification, and implementation of Boolean expressions much more systematic and easier.

### The Sum-of-Products (SOP) Form:

When two or more product terms are summed by Boolean addition, the resulting expression is a sum-of-products (SOP). Some examples are

$$AB + ABC$$

$$ABC + CDE + \overline{BCD}$$

$$\overline{AB} + \overline{ABC} + AC$$

## AND/OR Implementation of an SOP Expression

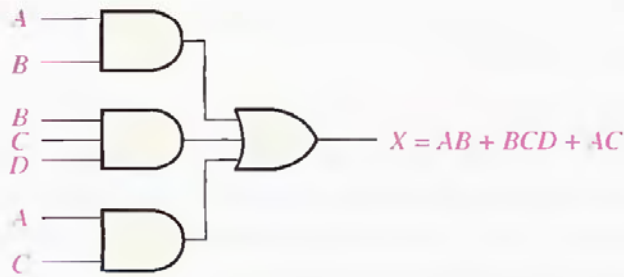


FIGURE 4-18

Implementation of the SOP expression  $AB + BCD + AC$ .

## NAND/NAND Implementation of an SOP Expression

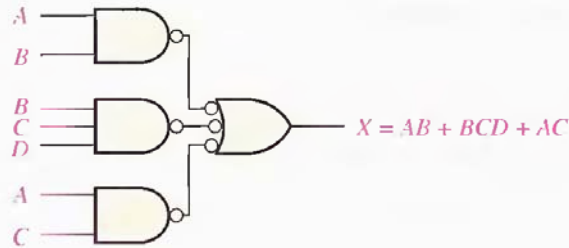


FIGURE 4-19

This NAND/NAND implementation is equivalent to the AND/OR in Figure 4-18.

## Conversion of a General Expression to SOP Form

Any logic expression can be changed into SOP form by applying Boolean algebra techniques. For example, the expression  $A(B + CD)$  can be converted to SOP form by applying the distributive law:

$$A(B + CD) = AB + ACD$$

### EXAMPLE 4-12

Convert each of the following Boolean expressions to SOP form:

(a)  $AB + B(CD + EF)$       (b)  $(A + B)(B + C + D)$       (c)  $\overline{(\overline{A} + \overline{B})} + C$

**Solution** (a)  $AB + B(CD + EF) = AB + BCD + BEF$

(b)  $(A + B)(B + C + D) = AB + AC + AD + BB + BC + BD$

(c)  $\overline{(\overline{A} + \overline{B})} + C = \overline{(\overline{A} + \overline{B})}\overline{C} = (A + B)\overline{C} = A\overline{C} + B\overline{C}$

**Related Problem** Convert  $\overline{A}B\overline{C} + (A + \overline{B})(B + \overline{C} + A\overline{B})$  to SOP form.